

گزارش تمرین vhdl سری 2 معماری کامپیوتر


آنوشا شریعتی 9923041

ماژول cas و تست بنچ :

طبق مدار داده شده در صورت سوال ماژول به شکل روبه رو طراحی شد. برای طراحی به یک بلوک فول ادر نیز نیاز داشتیم ولی برای راحتی کار به صورت ماژول جدا تعریف نشد و با توجه به مدار آن و با تعریف سیگنال t کد آن نوشته شد.

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity cas is
5     Port ( x : in  STD_LOGIC;
6           d : in  STD_LOGIC;
7           p : in  STD_LOGIC;
8           cin : in  STD_LOGIC;
9           r : out STD_LOGIC;
10          cout : out STD_LOGIC);
11 end cas;
12
13 architecture Behavioral of cas is
14
15     signal t : STD_LOGIC;
16
17 begin
18
19     t <= d xor p;
20     r <= t xor x xor cin ;           --full adder sum
21     cout <= (t or x) and (t or cin) and (x or cin) ; --full adder carry
22
23 end Behavioral;
24
```

```
55     wait for 100 ps;
56     x <= '1';
57     d <='0';
58     p <= '1';
59     cin <= '1';
60     wait for 100 ps;
61     x <= '0';
62     d <='0';
63     p <= '0';
64     cin <= '1';
65     wait for 100 ps;
66     x <= '0';
67     d <='0';
68     p <= '1';
69     cin <= '1';
70     wait for 100 ps;
71     x <= '1';
72     d <='1';
73     p <= '1';
74     cin <= '1';
75     wait for 100 ps;
76     x <= '1';
77     d <='0';
78     p <= '0';
79     cin <= '0';
```

 

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of 4 input LUTs	2	7,168	1%	
Number of occupied Slices	1	3,584	1%	
Number of Slices containing only related logic	1	1	100%	
Number of Slices containing unrelated logic	0	1	0%	
Total Number of 4 input LUTs	2	7,168	1%	
Number of bonded IOBs	6	141	4%	
Average Fanout of Non-Clock Nets	1.67			

ماژول x :

برای طراحی این ماژول از ماژول cas که در قسمت قبل توضیح داده شد به صورت component استفاده کردیم. سپس با استفاده از شکل مدار داده شده در صورت سوال با دستور port map ورودی و خروجی های ماژول cas را مشخص میکنیم.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity x_block is
5      Port ( a0 : in  STD_LOGIC;
6            a1 : in  STD_LOGIC;
7            a2 : in  STD_LOGIC;
8            a3 : in  STD_LOGIC;
9            a4 : in  STD_LOGIC;
10           dil : in  STD_LOGIC;
11           pil : in  STD_LOGIC;
12           pi2 : in  STD_LOGIC;
13           col : out STD_LOGIC;
14           co2 : out STD_LOGIC;
15           dol : out STD_LOGIC;
16           do2 : out STD_LOGIC;
17           r0 : out STD_LOGIC;
18           r1 : out STD_LOGIC;
19           r2 : out STD_LOGIC;
20           r3 : out STD_LOGIC;
21           r4 : out STD_LOGIC );
22 end x_block;
23
24 architecture Behavioral of x_block is
25
26     component cas is
27         Port ( x : in  STD_LOGIC;
28               d : in  STD_LOGIC;
29               p : in  STD_LOGIC;
30               cin : in  STD_LOGIC;
31               r : out STD_LOGIC;
32               cout : out STD_LOGIC);
33     end component;
34
35     signal npil : STD_LOGIC;
36     signal npil2 : STD_LOGIC;
37     signal t : STD_LOGIC_VECTOR (4 downto 0);
38     signal o : STD_LOGIC_VECTOR (1 downto 0);
39
40     begin
41         npil <= not pil;
42         npil2 <= not pi2;
43
44         cas_a : cas port map (
45             x => a0,
46             d => pil,
47             p=> pil,
48             cin => t(1),
49             r => r0,
50             cout => col
51         );
52
53         cas_b : cas port map (
54             x => a1,
55             d => npil,
56             p=> pil,
57             cin => t(0),
58             r => o(1),
59             cout => t(1)
60         );
61
62         cas_c : cas port map (
63             x => a2,
64             d => '1',
65             p=> pil,
66             cin => pil,
67             r => o(0),
68             cout => t(0)
69         );
70
71         cas_d : cas port map (
72             x => o(1),
73             d => dil,
74             p=> pi2,
75             cin => t(4) ,
76             r => r1,
77             cout => co2
78         );
79
80         cas_e : cas port map (
81             x => o(0),
82             d => pi2,
83             p=> pi2,
84             cin => t(3),
85             r => r2,
86             cout => t(4)
87         );
88
89         cas_f : cas port map (
90             x => a3,
91             d => npil2,
92             p=> pi2,
93             cin => t(2),
94             r => r3,
95             cout => t(3)
96         );
97
98         cas_g : cas port map (
99             x => a4,
100            d => '1',
101            p=> pi2,
102            cin => pi2,
103            r => r4,
104            cout => t(2)
105        );
106
107        do2 <= pi2 ;
108        dol <= dil ;
109
110    end Behavioral;
```

تست بنچ مارکول x :

```

85      wait for 100 ps;
86      a0 <= '1';
87      a1 <= '0';
88      a2 <= '0';
89      a3 <= '1';
90      a4 <= '1';
91      di1 <= '0';
92      pi1 <= '1';
93      pi2 <= '1';
94      wait for 100 ps;
95      a0 <= '0';
96      a1 <= '1';
97      a2 <= '1';
98      a3 <= '0';
99      a4 <= '0';
100     di1 <= '1';
101     pi1 <= '1';
102     pi2 <= '0';
103     wait for 100 ps;
104     a0 <= '1';
105     a1 <= '1';
106     a2 <= '0';
107     a3 <= '0';
108     a4 <= '0';
109     di1 <= '1';
110     pi1 <= '1';
111     pi2 <= '0';
112     wait for 100 ps;

```

```

112     wait for 100 ps;
113     a0 <= '1';
114     a1 <= '0';
115     a2 <= '1';
116     a3 <= '0';
117     a4 <= '1';
118     di1 <= '1';
119     pi1 <= '1';
120     pi2 <= '1';
121
122
123

```



سطوح مصرف:

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of 4 input LUTs	2	7,168	1%	
Number of occupied Slices	1	3,584	1%	
Number of Slices containing only related logic	1	1	100%	
Number of Slices containing unrelated logic	0	1	0%	
Total Number of 4 input LUTs	2	7,168	1%	
Number of bonded IOBs	6	141	4%	
Average Fanout of Non-Clock Nets	1.67			

ماژول y :

برای طراحی این ماژول مانند ماژول x از بلوک cas استفاده کردیم و با استفاده از شکل مدار خروجی و ورودی های آن را تعیین کردیم.

```
1  library IEEE;
2  use IEEE.STD_LOGIC_1164.ALL;
3
4  entity y_block is
5      Port ( dil : in  STD_LOGIC;
6            di2 : in  STD_LOGIC;
7            all : in  STD_LOGIC;
8            al2 : in  STD_LOGIC;
9            pil : in  STD_LOGIC;
10           pi2 : in  STD_LOGIC;
11           cil : in  STD_LOGIC;
12           ci2 : in  STD_LOGIC;
13           a22 : in  STD_LOGIC;
14           col : out STD_LOGIC;
15           co2 : out STD_LOGIC;
16           s11 : out STD_LOGIC;
17           s22 : out STD_LOGIC;
18           s21 : out STD_LOGIC;
19           do2 : out STD_LOGIC;
20           dol : out STD_LOGIC;
21           po2 : out STD_LOGIC;
22           pol : out STD_LOGIC);
23 end y_block;
24
25 architecture Behavioral of y_block is
26
27     component cas is
28         Port ( x : in  STD_LOGIC;
29               d : in  STD_LOGIC;
30               p : in  STD_LOGIC;
31               cin : in  STD_LOGIC;
32               r : out STD_LOGIC;
33               cout : out STD_LOGIC);
34     end component;
```

```
35
36     signal t : STD_LOGIC_VECTOR (1 downto 0);
37     signal o : STD_LOGIC;
38
39     begin
40
41     cas_h : cas port map (
42         x => all,
43         d => dil,
44         p=> pil,
45         cin => t(0),
46         r => s11,
47         cout => col
48     );
49
50     cas_i : cas port map (
51         x => al2,
52         d => di2,
53         p=> pil,
54         cin => cil,
55         r => o,
56         cout => t(0)
57     );
58
59     cas_j : cas port map (
60         x => o,
61         d => dil,
62         p=> pi2,
63         cin => t(1),
64         r => s21,
65         cout => co2
66     );
67
68     cas_k : cas port map (
69         x => a22,
70         d => di2,
71         p=> pi2,
72         cin => ci2,
73         r => s22 ,
74         cout => t(1)
75     );
76
77     pol <= pil;
78     po2 <= pi2;
79     dol <= dil;
80     do2 <= di2 ;
81
82
83
84
85 end Behavioral;
86
```

تست بنچ مائزول y :

```

90  -- hold reset state for 100 ns.
91  wait for 100 ps;
92      di1 <='1';
93      di2 <='1';
94      a11 <='0';
95      a12 <='0';
96      pi1 <='0';
97      pi2 <='0';
98      ci1 <='1';
99      ci2 <='1';
100     a22 <='1';
101  wait for 100 ps;
102      di1 <='1';
103      di2 <='1';
104      a11 <='0';
105      a12 <='1';
106      pi1 <='1';
107      pi2 <='1';
108      ci1 <='0';
109      ci2 <='0';
110     a22 <='0';
111  wait for 100 ps;
112      di1 <='0';
113      di2 <='1';
114      a11 <='1';
115      a12 <='0';
116      pi1 <='1';
117      pi2 <='0';
118      ci1 <='1';
119      ci2 <='0';
120     a22 <='1';

```



سطوح مصرف:

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of 4 input LUTs	8	7,168	1%	
Number of occupied Slices	5	3,584	1%	
Number of Slices containing only related logic	5	5	100%	
Number of Slices containing unrelated logic	0	5	0%	
Total Number of 4 input LUTs	8	7,168	1%	
Number of bonded IOBs	18	141	12%	
Average Fanout of Non-Clock Nets	2.41			

کد اصلی:

برای نوشتن کد اصلی از دو بلاک x,y که در قسمت قبل تعریف شد به صورت component استفاده میکنیم. سپس سیگنال های زیر را برای ارتباط بین ماژول ها تعریف میکنیم. سپس با دستور پورت مپ برای هر ماژول استفاده شده ورودی و خروجی ها را طبق شکل تعیین میکنیم. (کد خلاصه شده طبقه آخر)

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3
4 entity main_root is
5     Port ( input : in  STD_LOGIC_VECTOR (15 downto 0);
6           output : inout STD_LOGIC_VECTOR (7 downto 0));
7 end main_root;
8
9 architecture Behavioral of main_root is
10
11     component x_block is
12         Port ( a0 : in  STD_LOGIC;
13               a1 : in  STD_LOGIC;
14               a2 : in  STD_LOGIC;
15               a3 : in  STD_LOGIC;
16               a4 : in  STD_LOGIC;
17               di1 : in  STD_LOGIC;
18               pi1 : in  STD_LOGIC;
19               pi2 : in  STD_LOGIC;
20               co1 : out STD_LOGIC;
21               co2 : out STD_LOGIC;
22               do1 : out STD_LOGIC;
23               do2 : out STD_LOGIC;
24               r0 : out STD_LOGIC;
25               r1 : out STD_LOGIC;
26               r2 : out STD_LOGIC;
27               r3 : out STD_LOGIC;
28               r4 : out STD_LOGIC);
29     end component;
30
31     Port ( di1 : in  STD_LOGIC;
32           di2 : in  STD_LOGIC;
33           a11 : in  STD_LOGIC;
34           a12 : in  STD_LOGIC;
35           pi1 : in  STD_LOGIC;
36           pi2 : in  STD_LOGIC;
37           ci1 : in  STD_LOGIC;
38           ci2 : in  STD_LOGIC;
39           a22 : in  STD_LOGIC;
40           co1 : out STD_LOGIC;
41           co2 : out STD_LOGIC;
42           s11 : out STD_LOGIC;
43           s22 : out STD_LOGIC;
44           s21 : out STD_LOGIC;
45           do2 : out STD_LOGIC;
46           do1 : out STD_LOGIC;
47           po2 : out STD_LOGIC;
48           po1 : out STD_LOGIC);
49     end component;
50
51     signal o1 : STD_LOGIC_VECTOR (4 downto 0); --vertical outputs of first level
52     signal o2 : STD_LOGIC_VECTOR (8 downto 0); --vertical outputs of second level
53     signal o3 : STD_LOGIC_VECTOR (12 downto 0); --vertical outputs of third level
54     --left to right outputs
55     signal h2 : STD_LOGIC_VECTOR (1 downto 0); --horizontal outputs of second level
56     signal h3 : STD_LOGIC_VECTOR (3 downto 0); --horizontal outputs of third level
57     signal h4 : STD_LOGIC_VECTOR (5 downto 0); --horizontal outputs of fourth level
58     --right to left outputs
59     signal m2 : STD_LOGIC_VECTOR (2 downto 0); --horizontal outputs of second level
60     signal m3 : STD_LOGIC_VECTOR (5 downto 0); --horizontal outputs of third level
61
62     signal m4 : STD_LOGIC_VECTOR (8 downto 0);
63
64     signal r : STD_LOGIC_VECTOR (16 downto 0);
65     signal a : STD_LOGIC_VECTOR (16 downto 1);
66     signal q : std_logic_vector(8 downto 1);
67
68     begin
69
70     a(1)<= input(15);
71     a(2)<= input(14);
72     a(3)<= input(13);
73     a(4)<= input(12);
74     a(5)<= input(11);
75     a(6)<= input(10);
76     a(7)<= input(9);
77     a(8)<= input(8);
78     a(9)<= input(7);
79     a(10)<= input(6);
80     a(11)<= input(5);
81     a(12)<= input(4);
82     a(13)<= input(3);
83     a(14)<= input(2);
84     a(15)<= input(1);
85     a(16)<= input(0);
```



```

216 --fourth level
217
218 y4 : y_block port map (
219     di1 => o3(0),
220     di2 => o3(1),
221     a11 => o3(2),
222     a12 => o3(4),
223     pi1 => q(6),
224     pi2 => q(7),
225     ci1 => m4(6),
226     ci2 => m4(8),
227     a22 => m4(7),
228     co1 => q(7),
229     co2 => q(8),
230     --s11 => nc,
231     s22 => R(8),
232     s21 => R(7),
233     --do2 => nc,
234     --dol => nc,
235     po2 => h4(1),
236     pol => h4(0)
237 );
238
239 y5 : y_block port map (
240     di1 => o3(3),
241     di2 => o3(5),
242     a11 => o3(6),
243     a12 => o3(8),
244     pi1 => h4(0),
245     pi2 => h4(1),
246     ci1 => m4(3),
247     ci2 => m4(5),
248     a22 => m4(4),

```

```

249     col => m4(6),
250     co2 => m4(8),
251     s11 => m4(7),
252     s22 => r(10),
253     s21 => r(9),
254     --do2 => nc,
255     --dol => nc,
256     po2 => h4(3),
257     pol => h4(2)
258 );
259 y6 : y_block port map (
260     di1 => o3(7),
261     di2 => o3(9),
262     a11 => o3(10),
263     a12 => o3(11),
264     pi1 => h4(2),
265     pi2 => h4(3),
266     ci1 => m4(0),
267     ci2 => m4(2),
268     a22 => m4(1),
269     co1 => m4(3),
270     co2 => m4(5),
271     s11 => m4(4),
272     s22 => r(12),
273     s21 => r(11),
274     --do2 => nc,
275     --dol => nc,
276     po2 => h4(5),
277     pol => h4(4)
278 );
279

```




```



280 x4 : x_block port map (
281     a0 => o3(11),
282     a1 => a(13),
283     a2 => a(14),
284     a3 => a(15),
285     a4 => a(16),
286     di1 => h4(4),
287     pi1 => h4(4),
288     pi2 => h4(5),
289     co1 => m4(0),
290     co2 => m4(2),
291     --dol => nc,
292     --do2 => nc,
293     r0 => m4(1),
294     r1 => r(13),
295     r2 => r(14),
296     r3 => r(15),
297     r4 => r(16)
298 );
299 output(0) <= q(8);
300 output(1) <= q(7);
301 output(2) <= q(6);
302 output(3) <= q(5);
303 output(4) <= q(4);
304 output(5) <= q(3);
305 output(6) <= q(2);
306 output(7) <= q(1);
307
308
309
310 end Behavioral;

```


آر تی ال شماتیک:

شماتیک بلوک cas و x و y داخل مدار کلی:

 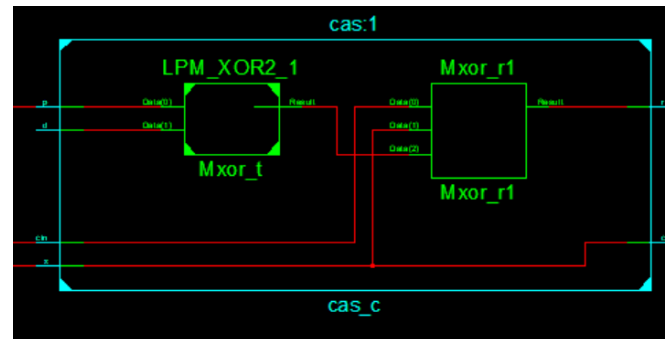 

  

تکنولوژی شماتیک:

 

سطوح مصرف:

Device Utilization Summary				
Logic Utilization	Used	Available	Utilization	Note(s)
Number of 4 input LUTs	69	7,168	1%	
Number of occupied Slices	37	3,584	1%	
Number of Slices containing only related logic	37	37	100%	
Number of Slices containing unrelated logic	0	37	0%	
Total Number of 4 input LUTs	69	7,168	1%	
Number of bonded IOBs	24	141	17%	
Average Fanout of Non-Clock Nets	3.02			

Timing constraint: Default path analysis
Total number of paths / destination ports: 542810 / 8

Delay: 52.881ns (Levels of Logic = 31)
Source: input<12> (PAD)
Destination: output<0> (PAD)

Data Path: input<12> to output<0>

Cell:in->out	fanout	Gate Delay	Net Delay	Logical Name (Net Name)
IBUF:I->O	7	0.821	1.405	input_12_IBUF (input_12_IBUF)
LUT3:I0->O	2	0.551	1.216	x2/cas_a/cout1 (m2<0>)
LUT4:I0->O	2	0.551	1.216	y1/cas_h/cout58_SW0 (N60)
LUT4:I0->O	10	0.551	1.329	y1/cas_h/cout58 (output_5_OBUF)
LUT4:I1->O	2	0.551	1.216	x2/cas_d/cout1 (m2<1>)
LUT3:I0->O	2	0.551	0.945	y1/cas_j/cout79_SW0 (N66)
LUT3:I2->O	2	0.551	0.903	y3/cas_i/Mxor_t_Result1 (y3/cas_i/t)
LUT4:I3->O	2	0.551	0.903	y3/cas_i/cout1 (y3/t<0>)
LUT4:I3->O	2	0.551	1.216	y3/cas_h/cout1 (m3<3>)
LUT3:I0->O	2	0.551	0.945	y2/cas_h/cout79_SW0 (N64)
LUT3:I2->O	10	0.551	1.329	y2/cas_h/cout79 (output_3_OBUF)
LUT4:I1->O	2	0.551	1.216	x3/cas_d/cout1 (m3<2>)
LUT4:I0->O	2	0.551	0.903	y3/cas_k/cout1 (y3/t<1>)
LUT4:I1->O	2	0.551	1.072	y3/cas_j/cout1 (m3<5>)
LUT3:I1->O	3	0.551	1.102	y2/cas_j/cout80_SW0 (N62)
LUT4:I1->O	1	0.551	0.827	y6/cas_i/cout_SW2 (N72)
LUT4:I3->O	2	0.551	0.903	y6/cas_i/cout (y6/t<0>)
LUT4:I3->O	3	0.551	1.246	y6/cas_h/cout1 (m4<3>)
LUT4:I0->O	1	0.551	1.140	y5/cas_i/cout1 (y5/t<0>)
LUT4:I0->O	3	0.551	0.975	y5/cas_h/cout1 (m4<6>)
LUT4:I2->O	1	0.551	0.000	y4/cas_h/cout89_F (N80)
MUXF5:I0->O	10	0.360	1.473	y4/cas_h/cout89 (output_1_OBUF)
LUT4:I3->O	3	0.551	1.246	y6/cas_h/cout1 (m4<3>)
LUT4:I0->O	1	0.551	1.140	y5/cas_i/cout1 (y5/t<0>)
LUT4:I0->O	3	0.551	0.975	y5/cas_h/cout1 (m4<6>)
LUT4:I2->O	1	0.551	0.000	y4/cas_h/cout89_F (N80)
MUXF5:I0->O	10	0.360	1.473	y4/cas_h/cout89 (output_1_OBUF)
LUT4:I0->O	1	0.551	0.827	x4/cas_d/cout (m4<2>)
LUT4:I3->O	1	0.551	0.827	y6/cas_k/cout (y6/t<1>)
LUT4:I3->O	1	0.551	0.996	y6/cas_j/cout (m4<5>)
LUT4:I1->O	1	0.551	0.827	y5/cas_j/cout70_SW0 (N68)
LUT4:I3->O	2	0.551	0.903	y5/cas_j/cout70 (m4<8>)
LUT4:I3->O	1	0.551	1.140	y4/cas_j/cout38 (y4/cas_j/cout38)
LUT4:I0->O	1	0.551	0.827	y4/cas_j/cout84_SW0 (N70)
LUT4:I3->O	1	0.551	0.801	y4/cas_j/cout94 (output_0_OBUF)
OBUF:I->O		5.644		output_0_OBUF (output<0>)
Total		52.881ns	(22.253ns logic, 30.628ns route)	(42.1% logic, 57.9% route)

Total REAL time to Xst completion: 8.00 secs
Total CPU time to Xst completion: 8.83 secs

-->

Total memory usage is 4513444 kilobytes

Number of errors : 0 (0 filtered)
Number of warnings : 18 (0 filtered)
Number of infos : 0 (0 filtered)

* Final Report *

Final Results
RTL Top Level Output File Name : main_root.ngc
Top Level Output File Name : main_root
Output Format : NGC
Optimization Goal : Speed
Keep Hierarchy : No

Design Statistics
IOs : 24
Cell Usage :
BELS : 70
LUT2 : 6
LUT3 : 19
LUT4 : 44
MUXF5 : 1
IO Buffers : 24
IBUF : 16
OBUF : 8

HDL Synthesis Report

Macro Statistics
Xors : 104
1-bit xor2 : 52
1-bit xor3 : 52

* Advanced HDL Synthesis *

Advanced HDL Synthesis Report

Macro Statistics
Xors : 104
1-bit xor2 : 52
1-bit xor3 : 52

Device utilization summary:

Selected Device : 3s400pq208-4

Number of Slices: 39 out of 3584 1%
Number of 4 input LUTs: 69 out of 7168 0%
Number of IOs: 24
Number of bonded IOBs: 24 out of 141 17%

کد تست بنچ و شبیه سازی:

```

29  //
30
31  stim_proc: process
32  begin
33
34      wait for 100 ps;           --the answer we expect in the tb
35      input <= "0000000000000001"; --output=1
36      wait for 100 ps;
37      input <= "0000000000010000"; --output=4
38      wait for 100 ps;
39      input <= "0000000101000100"; --output=18
40      wait for 100 ps;
41      input <= "0000001001110010"; --output=25
42      wait for 100 ps;
43      input <= "1010101010101010"; --output=208
44      wait for 100 ps;
45      input <= "0011001100010100"; --output=114
46      wait for 100 ps;
47
48
49

```

